# EE599 Assignment 2


Yihao Wang 7410-1780-57

Github Repo Link: https://github.com/KevinWang96/EE599\_YihaoWang\_7410178057.git


#### 1. Barrel Shifter

## 1.1 16 elements design

a. Schematic of elaborated design

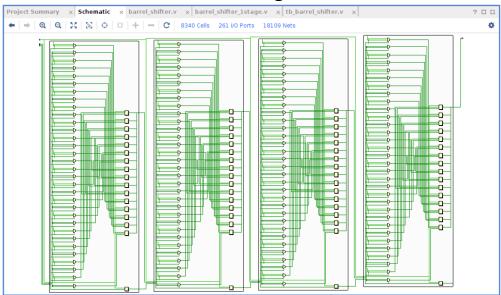


b. Schematic of synthesized design

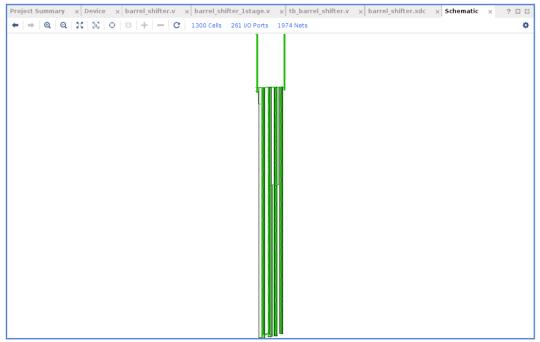


## c. Timing report (clock cycle is 10 ns)



#### d. Utilization report

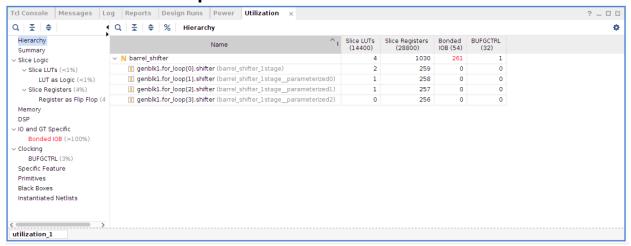


## e. Power report

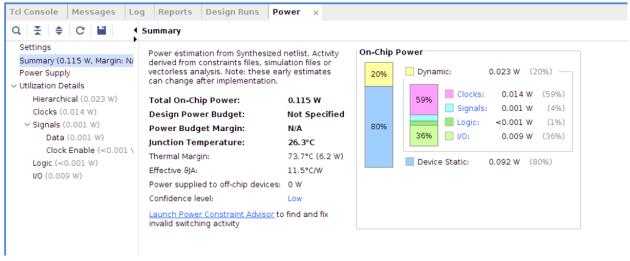


# 1.2 64 elements design

## a. Schematic of elaborated design

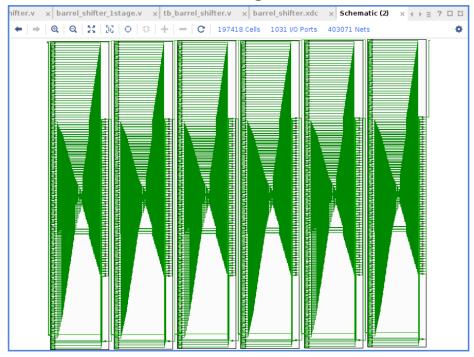


## b. Schematic of synthesized design

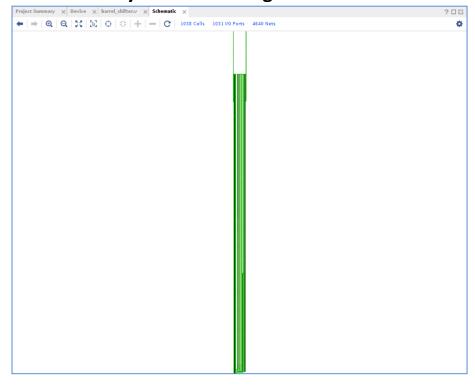


## c. Timing report (clock cycle is 10 ns)



### d. Utilization report

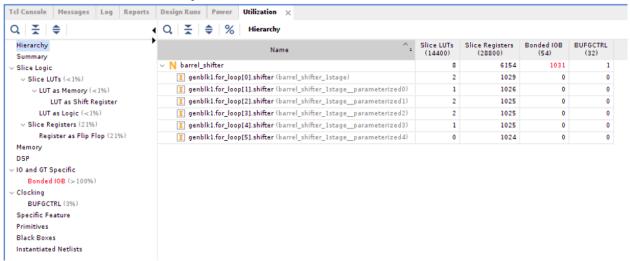

#### e. Power report

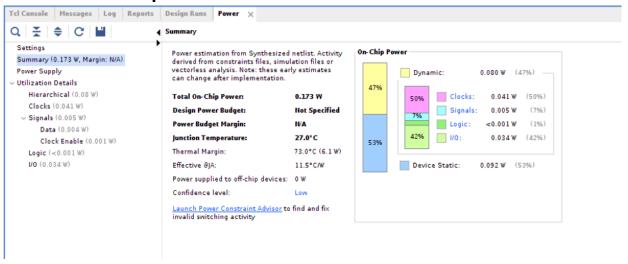


## 2. Systolic Array for Dense Matrix-Matrix Multiplication


## 2.1 16x16 design
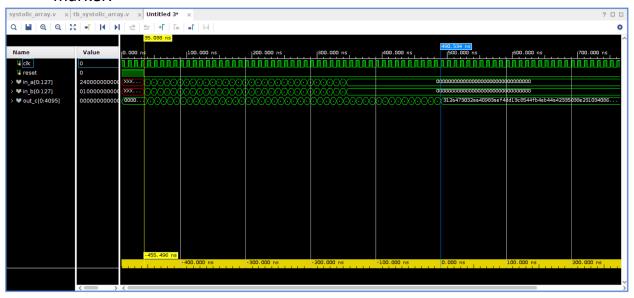
#### a. Waveform


The input stream starts at yellow marker and results come out at blue marker.




## b. Schematic of elaborated design

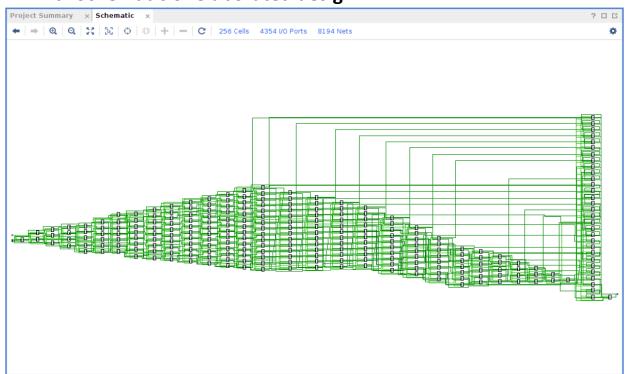


### c. Schematic of synthesized design

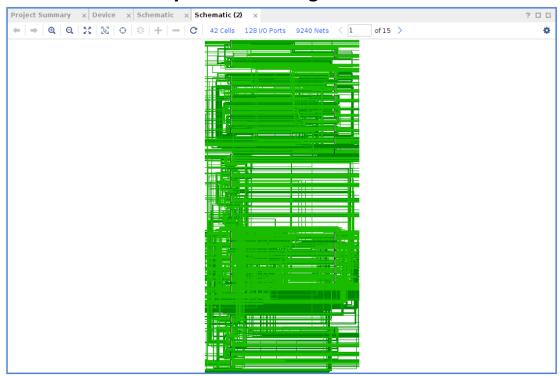

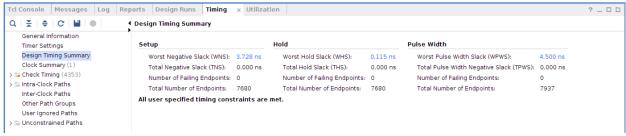
## d. Timing report (clock cycle is 10 ns)



### e. Utilization report

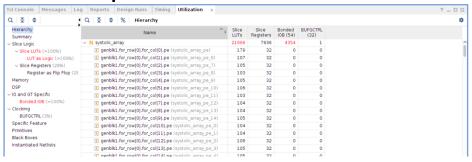


#### f. Power report

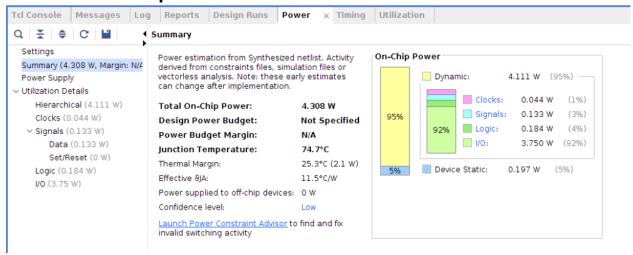


## 2.2 32x32 Design
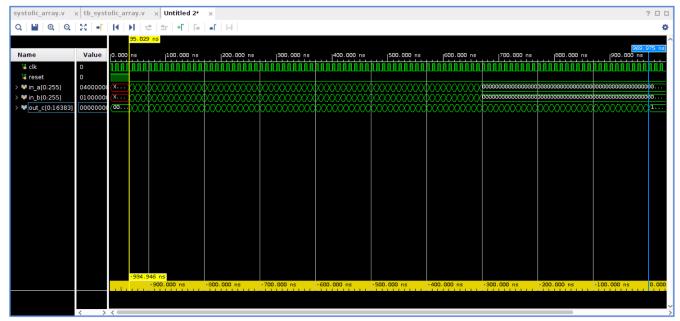
#### a. Waveform


The input stream starts at yellow marker and results come out at blue marker.



# b. Schematic of elaborated design

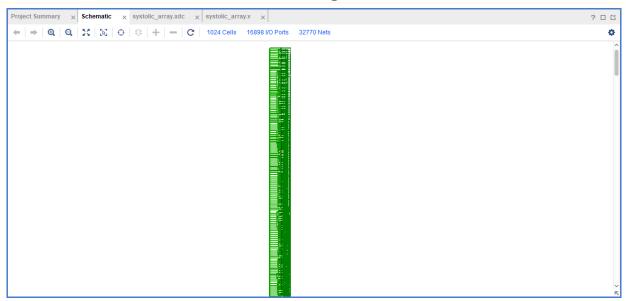


# c. Schematic of synthesized design

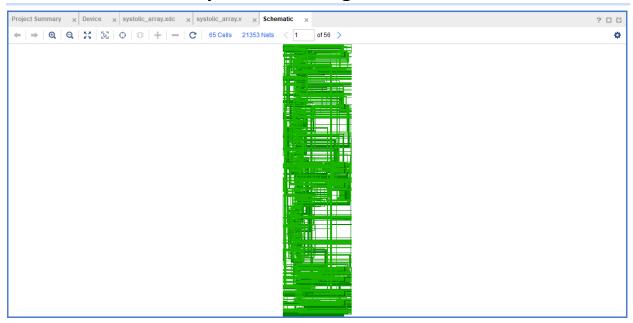

## d. Timing report (clock cycle is 10 ns)



## e. Utilization report

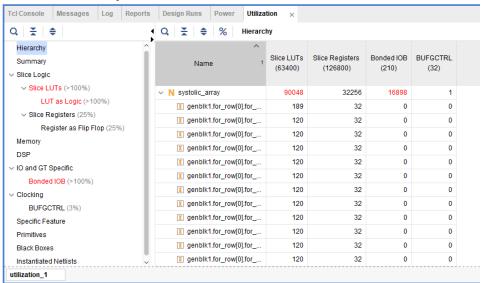

### f. Power report

